


Chapter - 4

FET BIASING


Contents

- Operating point
- Load line analysis
- Biasing
- Types of Biasing
- Fixed bias circuit
- Voltage divider bias circuit

 When a line is drawn joining the saturation and cut off points, such a line can be called as Load line. This line, when drawn over the output characteristic curve, makes contact at a point called as Operating point.



 a **load line** is a **line** drawn on the characteristic curve, a graph of the current vs. the voltage in a nonlinear device like a diode or transistor. It represents the constraint put on the voltage and current in the nonlinear device by the external circuit.



Introduction of Biasing

The analysis or design of a transistor amplifier requires knowledge of both the dc and ac response of the system. In fact, the amplifier increases the strength of a weak signal by transferring the energy from the applied DC source to the weak input ac signal. The analysis or design of any electronic amplifier therefore has two components:

- The dc portion and
- The ac portion During the design stage, the choice of parameters for the required dc levels will affect the ac response.

Biasing: Application of dc voltages to establish a fixed level of current and voltage.

Purpose of DC biasing circuit:


- To turn the device “ON”
- To place it in operation in the region of its characteristic where the device operates most linearly .
- Proper biasing circuit which it operate in linear region and circuit have centered Q-point or midpoint biased
- Improper biasing cause Improper biasing cause
- ☐ Distortion in the output signal
- ☐ Produce limited or clipped at output signal

Types of DC Biasing Circuits

- Fixed-bias circuit
- Emitter-stabilized bias circuit
- Collector-emitter loop
- Voltage divider bias circuit
- DC bias with voltage feedback

Fixed Base Bias Circuit

3

 


- This is common emitter (CE) configuration
- 1st step: Locate capacitors and replace them with an open circuit
- 2nd step: Locate 2 main loops which;
 - BE loop
 - CE loop

Fixed Base Bias Circuit

1

 
- 1st step: Locate capacitors and replace them with an open circuit



Fixed Base Bias Circuit


5

- 2nd step: Locate 2 main loops.

 

Fixed Base Bias Circuit

6

 

□ BE Loop Analysis


□ $V_{CC} - I_B R_B - V_{BE} = 0$

Therefore,

$$I_B = (V_{CC} - V_{BE}) / R_B$$

Fixed Base Bias Circuit

7

 

CE Loop Analysis

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\text{But } I_C = \beta I_B$$

$$V_{CE} = \beta_{DC} ((V_{CC} - V_{BE}) / R_B)$$

Fixed Base Bias Circuit




❑ DISADVANTAGE

- ❑ Unstable – because it is too dependent on β and produce width change of Q-point
- ❑ For improved bias stability , add emitter resistor to dc bias.

Voltage Divider Bias Circuit

3

 


- Provides good Q-point stability with a single polarity supply voltage
- 1st step: Locate capacitors and replace them with an open circuit
- 2nd step: Simplified circuit using Thevenin Theorem
- 3rd step: Locate 2 main loops which;
 - BE loop
 - CE loop

Voltage Divider Bias Circuit

1

 
- 1st step: Locate capacitors and replace them with an open circuit



Voltage Divider Bias Circuit

5

 - 2nd step: : Simplified circuit using **Thevenin Theorem**



From Thevenin Theorem;


$$R_{TH} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

Voltage Divider Bias Circuit

6


- 3rd step: : Locate 2 main loops.

 

Voltage Divider Bias Circuit

7

□ BE Loop Analysis

 

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

Recall; $I_E = (\beta + 1)I_B$

Substitute for I_E


$$V_{TH} - I_B R_{TH} - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E}$$

Voltage Divider Bias Circuit

8

□ CE Loop Analysis

 

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

Assume;

$$I_E \approx I_C$$

Therefore;

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$